




Question 1

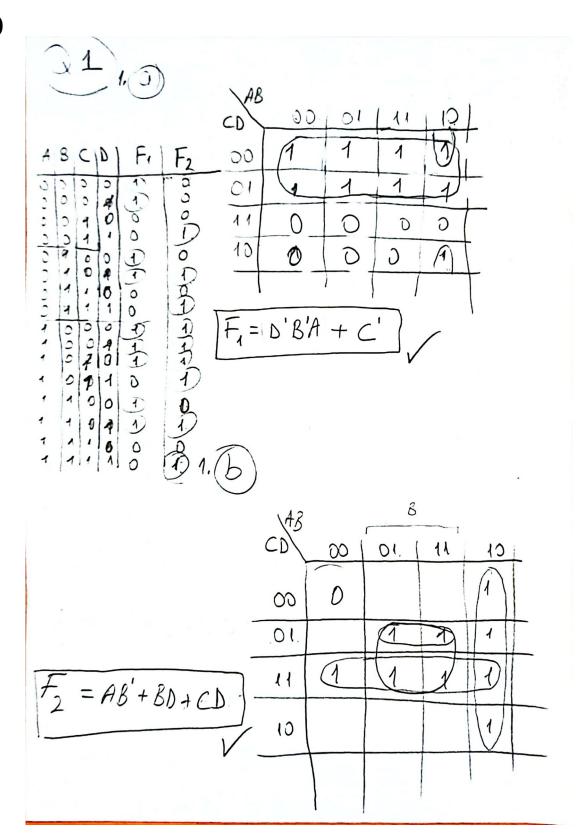

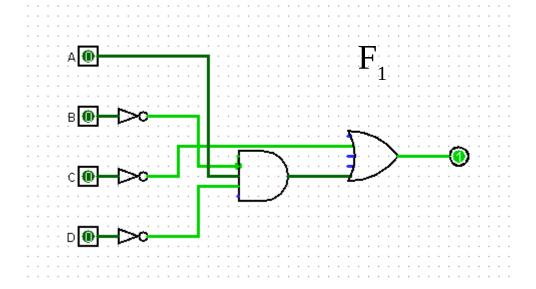

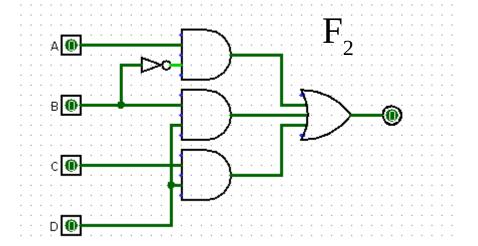

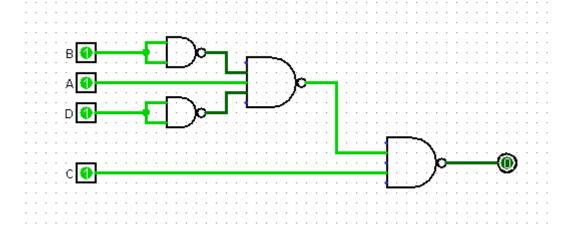

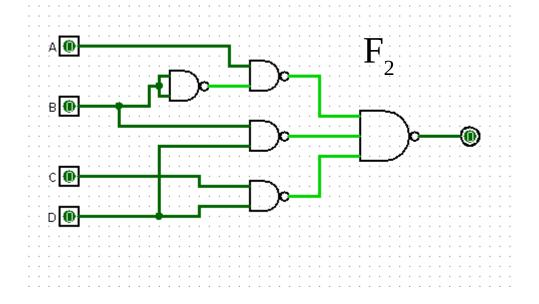

CSE 232 HW-2 Mehmet Hüseyin YILDIZ 200104004095

Question 2

1)

| A | В | С | D | F |
|---|---|---|---|---|
| 0 | 0 | 0 | 0 | 1 |
| 0 | 0 | 0 | 1 | 0 |
| 0 | 0 | 1 | 0 | 1 |
| 0 | 0 | 1 | 1 | 0 |
| 0 | 1 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 0 | 1 |
| 0 | 1 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 | 1 |
| 1 | 0 | 0 | 1 | 1 |
| 1 | 0 | 1 | 0 | 1 |
| 1 | 0 | 1 | 1 | 1 |
| 1 | 1 | 0 | 0 | 0 |
| 1 | 1 | 0 | 1 | 1 |
| 1 | 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 1 | 1 |

| _{CD} \ ^{AB} | 00 | 01 | 11 | 10 |
|-------------------------------|----|----|----|----|
| 00 | 1 | 0 | 0 | 1 |
| 01 | 0 | 0 | 1 | 1 |
| 11 | 0 | 1 | 1 | 1 |
| 10 | 1 | 1 | 1 | 1 |

| _{CD} \ ^{AB} | 00 | 01 | 11 | 10 |
|-------------------------------|----|----|----|----|
| 00 | 1 | 0 | 0 | 1 |
| 01 | 0 | 0 | 1 | 1 |
| 11 | 0 | 1 | 1 | 1 |
| 10 | 1) | 1 | 1 | |

$$F = AD + BC + B'D'$$

| _{CD} \ ^{AB} | 00 | 01 | 11 | 10 |
|-------------------------------|----|----|----|----|
| 00 | 1 | 0 | 0 | 1 |
| 01 | 0 | 0 | 1 | 1 |
| 11 | 0 | 1 | 1 | 1 |
| 10 | 1 | 1 | 1 | 1 |

$$F' = A'B'D + A'C'D + BC'D'$$

