

Step 2

- -> 7 states (3 bits resister)
- -) 3 lits for coming states
- -) X, y and 2 are outputs.

Step 3

		-	-	ALIEN PARTIES	
He	des	52	Si	So	
	A	0	0	0	
	B	0	0	1	
	C	0	1	0	
-	0	0	1	1	
	E	1	0	0	
	FI	1	0	1	
	G	1	1	10	-
	(!	ì	

Step 4

state	S ₂	S ₁	S ₀	a	Х	у	Z	n ₂	n ₁	n_0
Α	0	0	0	0	0	0	0	0	0	0
Α	0	0	0	1	0	0	0	0	0	1
В	0	0	1	0	0	1	1	0	0	1
В	0	0	1	1	0	1	1	0	1	0
С	0	1	0	0	1	1	1	0	1	0
С	0	1	0	1	1	1	1	0	1	1
D	0	1	1	0	0	1	0	0	1	1
D	0	1	1	1	0	1	0	1	0	0
E	1	0	0	0	0	0	1	1	0	0
Е	1	0	0	1	0	0	1	1	0	1
F	1	0	1	0	1	0	1	1	0	1
F	1	0	1	1	1	0	1	1	1	0
G	1	1	0	0	1	0	0	1	1	0
G	1	1	0	1	1	0	0	0	0	0
No	1	1	1	0						
No	1	1	1	1						

Step 5.1

$$x = S_{0}^{'}S_{1}S_{2}^{'} + S_{0}S_{1}^{'}S_{2} + S_{0}^{'}S_{1}S_{2} = S_{0}^{'}S_{1}\left(S_{2} + S_{2}^{'}\right) + S_{0}S_{1}^{'}S_{2}$$

$$x = S_{0}^{'}S_{1} + S_{0}S_{1}^{'}S_{2}$$

$$y = S_{2}^{'}S_{1}S_{0} + S_{2}^{'}S_{1}S_{0} = S_{2}^{'}S_{1}\left(S_{0}^{'} + S_{0}^{'}\right) + S_{2}^{'}S_{1}^{'}S_{0}$$

$$y = S_{2}^{'}\left(S_{1}^{'}S_{0} + S_{1}^{'}\right)$$

$$2 = S_{1}'S_{0}(S_{2}+S_{2}') + S_{0}'(S_{2}'S_{1}+S_{2}S_{1}')$$

$$2 = S_{1}'S_{0} + S_{0}'(S_{2}\oplus S_{1})$$


$$3 = S_{2}\oplus S_{1}$$

$$4 = S_{1}'S_{0} + S_{0}'(S_{2}\oplus S_{1})$$

$$n_2 = os_2's_4s_6 + s_2s_1's_6' + s_2s_1's_6 + o's_2s_4's_6'$$

$$n_2 = \left[s_1\left(os_2's_6 + o's_2s_6'\right) + s_2s_1'\right]\left(s_6 + s_6'\right)$$
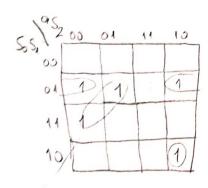
$$n_{4} = \alpha S_{2}' S_{1}' S_{0} + S_{2}' S_{1}' S_{0}' + \alpha' S_{2}' S_{1}' S_{0} + \alpha S_{2}' S_{1}' S_{0} + \alpha' S_{2}' S_{1}' S_{0}'$$



$$n_1 = S_0'S_1S_2' + OS_2'S_0S_1' + OS_1(S_0 \oplus S_2)$$

$$= o'S_{1} \left(S_{2} S_{0}' + o'S_{2}' S_{0} S_{1} \right)$$

$$= o'S_{1} \left(S_{2} S_{0}' + S_{2}' S_{0} \right)$$

$$= o'S_{1} \left(S_{0} \oplus S_{2} \right)$$

Step 5.2

